 


**ES 204: DIGITAL SYSTEMS**  
**TAKE HOME LAB ASSIGNMENT 5**

**DESIGNING AND IMPLEMENTING**  
**OF A TINY PROCESSOR**  
**USING VERILOG**



**SUBMITTED BY:**

ANIRUDH MITTAL (23110029)

ANURAG SINGH (23110035)

**TO:**

PROF. JOYCEE MEKIE (INSTRUCTOR)

ARNAV (T.A.)

## Question

Implementation of the Complete “Tiny” Processor Design, which runs one program. The following processor has a register file consisting of 16 registers, each of 8 bits. The processor can execute the following instructions. The instructions that need 2 operands will take one of the operands from the Register file and another from the accumulator. The result will be transferred to the Accumulator. There is an 8-bit extended (EXT) register used only during multiplication. This register stores the higher-order bits during multiplication and the quotient during division. The C/B register holds the carry and borrow during addition and subtraction, respectively.

1. Register bank is of 16 registers, each of 8 bits.
2. Accumulator, Program counter, etc., are different registers not connected with the bank
3. Branch and Return instructions update the Program counter with the address provided. (These two need not be used to make a code.)
4. The program is stored in memory, which you need to create in the design. Alternatively, you can give the instructions using a testbench.

The Instruction Set Table was given in the PDF.

## HELPER CODES FOR ALU UNIT

### Full Adder Module:

```
module full_adder(  
    input A,  
    input B,  
    input Cin,  
    output SUM,  
    output Cout  
);  
    assign SUM = A ^ B ^ Cin;  
    assign Cout = (A & B) | (B & Cin) | (Cin & A);  
endmodule
```

### Adder Module Combined:

```
module adder(  
    input [7:0] A,  
    input [7:0] B,  
    output [7:0] SUM,  
    output CARRY  
);  
    wire [7:0] carry;  
  
    full_adder FA0 (A[0], B[0], 1'b0, SUM[0], carry[0]);  
    full_adder FA1 (A[1], B[1], carry[0], SUM[1], carry[1]);  
    full_adder FA2 (A[2], B[2], carry[1], SUM[2], carry[2]);  
    full_adder FA3 (A[3], B[3], carry[2], SUM[3], carry[3]);  
    full_adder FA4 (A[4], B[4], carry[3], SUM[4], carry[4]);  
    full_adder FA5 (A[5], B[5], carry[4], SUM[5], carry[5]);  
    full_adder FA6 (A[6], B[6], carry[5], SUM[6], carry[6]);
```

```
full_adder FA7 (A[7], B[7], carry[6], SUM[7], carry[7]);
```

```
    assign CARRY = carry[7];  
endmodule
```

### **Subtractor Module:**

```
module subtractor(  
    input [7:0] A,  
    input [7:0] B,  
    output [7:0] DIFF,  
    output BORROW  
);  
    wire [7:0] B_complement;  
    wire [7:0] temp_sum;  
    wire carry;  
  
    // Take 2's complement of B => ~B + 1  
    assign B_complement = ~B;  
  
    // Use the same adder to compute A + (~B + 1)  
    adder ADDER(.A(A), .B(B_complement + 1'b1), .SUM(DIFF), .CARRY(carry));  
  
    assign BORROW = ~carry; // If carry is not generated, it was a borrow  
endmodule
```

### **Shifter Module:**

```
module shifter(D, clk, Q, mode);  
    parameter n = 8;  
    input [n-1:0] D;  
    input clk;  
    input [3:0] mode;  
    output reg [n-1:0] Q;  
  
    integer k;  
  
    // Mode parameters  
    parameter logical_right  = 4'b0010;  
    parameter arithmetic_right = 4'b0101;  
    parameter circular_left  = 4'b0100;  
    parameter circular_right = 4'b0011;  
    parameter logical_left   = 4'b0001;  
  
    always @(posedge clk)  
    begin  
        case (mode)  
            logical_right:  
                begin
```

```

        for (k = 0; k < n-1; k = k + 1)
            Q[k] <= Q[k+1];
        Q[n-1] <= 1'b0; // fill MSB with 0
    end

    arithmetic_right:
    begin
        for (k = 0; k < n-1; k = k + 1)
            Q[k] <= Q[k+1];
        Q[n-1] <= Q[n-1]; // preserve MSB
    end

    circular_left:
    begin
        for (k = n-1; k > 0; k = k - 1)
            Q[k] <= Q[k-1];
        Q[0] <= Q[n-1]; // wrap MSB to LSB
    end

    circular_right:
    begin
        for (k = 0; k < n-1; k = k + 1)
            Q[k] <= Q[k+1];
        Q[n-1] <= Q[0]; // wrap LSB to MSB
    end

    logical_left:
    begin
        for (k = n-1; k > 0; k = k - 1)
            Q[k] <= Q[k-1];
        Q[0] <= 1'b0; // fill LSB with 0
    end

    default:
        Q <= D; // load new data if mode is unknown
    endcase
end
endmodule

```

### **Comparator Module:**

```

module comparator(
    A, B, out
);
    input [7:0] A, B;
    output out;

    wire [7:0] X;
    assign X = A^B;

```

```
assign out = (A >= B) ? 1'b1 : 1'b0;
endmodule
```

### **Multiplier Module:**

```
module multiplier (
    input [7:0] A, // Multiplicand
    input [7:0] B, // Multiplier
    output [15:0] P // Product
);

    // Generate partial products pp[i][j] = A[j] AND B[i]
    wire [7:0] pp [7:0];
    genvar i, j;
    generate
        for (i = 0; i < 8; i = i + 1) begin : gen_pp_rows
            for (j = 0; j < 8; j = j + 1) begin : gen_pp_bits
                assign pp[i][j] = A[j] & B[i];
            end
        end
    endgenerate

    // Shift partial products to align
    wire [15:0] pp_sh [7:0];
    genvar k;
    generate
        for (k = 0; k < 8; k = k + 1) begin : gen_shift
            assign pp_sh[k] = {{8{1'b0}}, pp[k]} << k;
        end
    endgenerate

    // Iteratively add shifted partial products using 8-bit adder module
    wire [15:0] sum_arr [7:0];
    wire carry_lo [7:0];
    wire carry_hi [7:0];

    assign sum_arr[0] = pp_sh[0];

    generate
        for (k = 1; k < 8; k = k + 1) begin : gen_add
            // Lower 8 bits addition
            adder add_lo (
                .A(sum_arr[k-1][7:0]),
                .B(pp_sh[k][7:0]),
                .SUM(sum_arr[k][7:0]),
                .CARRY(carry_lo[k])
            );
            // Upper 8 bits addition with carry
            adder add_hi (
```

```

        .A(sum_arr[k-1][15:8]),
        .B(pp_sh[k][15:8]),
        .SUM(sum_arr[k][15:8]),
        .CARRY(carry_hi[k])
    );
end
endgenerate

```

```

// Final product is sum_arr[7]
assign P = sum_arr[7];

```

```
endmodule
```

### **Increment Module [uses adder]:**

```

module adder(
    input [7:0] A,
    input [7:0] B,
    output [7:0] SUM,
    output CARRY
);
    wire [7:0] carry;

    full_adder FA0 (A[0], B[0], 1'b0, SUM[0], carry[0]);
    full_adder FA1 (A[1], B[1], carry[0], SUM[1], carry[1]);
    full_adder FA2 (A[2], B[2], carry[1], SUM[2], carry[2]);
    full_adder FA3 (A[3], B[3], carry[2], SUM[3], carry[3]);
    full_adder FA4 (A[4], B[4], carry[3], SUM[4], carry[4]);
    full_adder FA5 (A[5], B[5], carry[4], SUM[5], carry[5]);
    full_adder FA6 (A[6], B[6], carry[5], SUM[6], carry[6]);
    full_adder FA7 (A[7], B[7], carry[6], SUM[7], carry[7]);

    assign CARRY = carry[7];
endmodule

```

### **Decrement Module [uses subtractor]:**

```

module subtractor(
    input [7:0] A,
    input [7:0] B,
    output [7:0] DIFF,
    output BORROW
);
    wire [7:0] B_complement;
    wire [7:0] temp_sum;
    wire carry;
    assign B_complement = ~B;
    adder ADDER(.A(A), .B(B_complement + 1'b1), .SUM(DIFF), .CARRY(carry));

```

```
    assign BORROW = ~carry;
endmodule
```

## **SEPARATE MODULE CODES**

### **Memory Module:**

```
module memory(data_in, clk, data_out, address, write);

input [7:0]data_in; // writing 8-bit data input to the memory
input write; // enable signal
// enables 1 for writing to memory and 0 for read only

input clk;
input [3:0]address; // 4-bit address
output [7:0]data_out;
reg [7:0] memo [0:15];

assign data_out = memo[address]; // The value written at that address is extracted from the memory
always@(posedge clk)
begin
    if (write) // enabling the write logic
        memo[address] = data_in;
end
endmodule
```

### **Instruction Memory Module:**

```
module instruction_memory(
    input [3:0] address, // 4-bit address from PC
    output reg [7:0] instruct // 8-bit instruction output extracting from memory
);

// writing the 16 bytes (each 8 bits) of the instruction memory, which
// stores 16 sets of instructions where each instruction is an 8-bit value
reg [7:0] memory [0:15];

// Initializing memory with all set of instructions
initial begin
    memory[0] = 8'b0000_0000; // NOP No operation
    memory[1] = 8'b0001_0001; // ADD R1 Add value in register R1 to accumulator
    memory[2] = 8'b0010_0010; // SUB R2 Subtract value in R2 from accumulator
    memory[3] = 8'b0011_0011; // MUL R3 Multiply accumulator with value in R3
    memory[4] = 8'b0101_0100; // AND R4 Bitwise AND with R4
    memory[5] = 8'b0110_0101; // XRA R5 Bitwise XOR with R5
end
```

```

memory[6] = 8'b0111_0110; // CMP R6   Compare accumulator with R6
memory[7] = 8'b0000_0001; // LSL ACC  Logical shift left accumulator
memory[8] = 8'b0000_0010; // LSR ACC  Logical shift right accumulator
memory[9] = 8'b0000_0011; // CIR ACC  Circular right shift accumulator
memory[10] = 8'b0000_0100; // CIL ACC  Circular left shift accumulator
memory[11] = 8'b0000_0101; // ASR ACC  Arithmetic shift right accumulator
memory[12] = 8'b0000_0110; // INC ACC  Increment accumulator
memory[13] = 8'b0000_0111; // DEC ACC  Decrement accumulator
memory[14] = 8'b1000_0010; // Br 12   Branch to address 2
memory[15] = 8'b1111_1111; // HLT    Halt the processor
end

```

```

// Output instruction at the given address
always @(*) begin
    instruct = memory[address];
end

```

```
endmodule
```

### **Arithmetic Logic Unit Module:**

```

module ALU(opcode, acc, data_reg, clk, acc_out, ext, cb);

input [7:0] opcode; // 8-bit operation code
input [7:0] acc, data_reg;
input clk;
output reg [7:0] acc_out, ext; // defining accumulator output and extended result of multiplier
output reg cb; // defining borrow carry

// Intermediate wires to hold outputs of operations
wire [7:0] add_res, sub_res, and_res, xra_res, shift_res, mul_lower, mul_upper, inc_res, dec_res;
wire add_c, sub_b, comp, inc_c, dec_b;

// Instantiating Operation modules as defined earlier

adder ADD(acc, data_reg, add_res, add_c); // Performs accumulator + data_reg
subtractor SUB(acc, data_reg, sub_res, sub_b); // Performs accumulator - data_reg
assign and_res = acc & data_reg; // Bitwise AND
assign xra_res = acc ^ data_reg; // Bitwise XOR
shifter SHIFT(acc, clk, shift_res, opcode[3:0]); // Shift operation
comparator COMP(acc, data_reg, comp); // Comparison
multiplier MUL(acc, data_reg, {mul_upper, mul_lower}); // Multiplies accumulator * data_reg
adder inc(acc, 1, inc_res, inc_c); // Increments accumulator by 1
subtractor dec(acc, 1, dec_res, dec_b); // Decrements accumulator by 1

always @(*)
begin

```



```

// Default values
acc_out = 8'b0;
ext = 8'b0;
cb = 1'b0;

// Choosing operation based on the opcode
casez (opcode)
  8'b0001_????:
  begin
    acc_out = add_res; // ADD
    cb = add_c; // Set carry flag
  end
  8'b0010_????:
  begin
    acc_out = sub_res; // SUB
    cb = sub_b; // Set borrow flag
  end
  8'b0011_????: // MUL
  begin
    acc_out = mul_lower; // Lower 8 bits of result
    ext = mul_upper; // Upper 8 bits of result
  end
// Shift instructions
  8'b0000_0001:
  begin
    acc_out = shift_res; // Left shift
  end
  8'b0000_0010:
  begin
    acc_out = shift_res; // Right shift
  end
  8'b0000_0011:
  begin
    acc_out = shift_res; // Circular Right
  end
  8'b0000_0100:
  begin
    acc_out = shift_res; // Circular Left
  end
  8'b0000_0101:
  begin
    acc_out = shift_res; // Arithmetic Right Shift
  end
  8'b0101_????:
  begin
    acc_out = and_res; // AND
  end
  8'b0110_????:
  begin
    acc_out = xra_res; // XOR

```

```

end
8'b0111_???:
begin
    acc_out = comp; // COMPARE
end
8'b0000_0110:
begin
    acc_out = inc_res; // Increment
    cb = inc_c; // Carry from increment
end
8'b0000_0111: // Decrement
begin
    acc_out = dec_res;
    cb = dec_b; // Borrow from decrement
end

default:
begin
    acc_out = acc;
end
endcase

end
endmodule

```

## **Main Processor Module**

```

module Processor(input clk, input rst);
    // defining wires for different units
    wire [3:0] pc; // program counter output
    wire [7:0] opcode; // operational code instruction taken from memory

    // last 4-bit address taken from the opcode to fetch the register from the register bank
    // as opcode is YYYY XXXX format where YYYY is instruction and XXXX is register address
    wire [3:0] add = opcode[3:0];

    wire [7:0] data_reg; // data from register file
    wire [3:0] pc_next = pc + 1; // updating the value of program counter

    reg pc_l; // enabling PC load
    reg [3:0] pc_in; // Program counter input value
    program_counter prct(
        .clk(clk),
        .rst(rst),
        .load(pc_l),
        .pc_in(pc_in),
        .pc_out(pc)
    );

```

```

// Calling Instruction Memory
// Extracting the instruction from the memory using the PC address
instruction_memory inst_mem(
    .address(pc),
    .instruct(opcode)
);

// Register File
reg [7:0] data_in; // Data value
reg write; // Signal to control the writing of data
memory reg_file(
    .data_in(data_in),
    .data_out(data_reg),
    .address(add),
    .write(write)
);

// Calling Internal Registers
reg [7:0] acc; // Accumulator register
reg [7:0] ext; // External Register
reg cb; // Borrow Carry Register
reg acc_ld, ext_ld, cb_ld; // Control signal for internal signals

// ALU outputs
wire [7:0] alu_acc_out; // Output which will be stored in accumulator
wire [7:0] alu_ext_out; // Output which will be stored in accumulator
wire alu_cb_out; // Output which will be stored in the accumulator

ALU alu(.opcode(opcode), .acc(acc), .data_reg(data_reg), .clk(clk), .acc_out(alu_acc_out),
.ext(alu_ext_out), .cb(alu_cb_out));

reg [7:0] acc_next_value; // Accumulator value to be taken in next clock cycle

// Combinational control logic
always @(*) begin
    // Default values
    acc_ld = 0;
    ext_ld = 0;
    cb_ld = 0;
    write = 0;
    data_in = 8'h00;
    pc_l = 1;
    pc_in = pc_next;
    acc_next_value = alu_acc_out;

// Decoding Instructions
casez (opcode)
    // NOP
    8'b0000_0000: ;
    // ADD

```

```

8'b0001_????: begin acc_ld=1; cb_ld=1; end
// SUB
8'b0010_????: begin acc_ld=1; cb_ld=1; end
// MUL
8'b0011_????: begin acc_ld=1; ext_ld=1; end
// ASR
8'b0000_0001,
8'b0000_0010,
8'b0000_0011,
8'b0000_0100,
8'b0000_0101: begin acc_ld=1; end
// XOR
8'b0110_????: begin acc_ld=1; end
// Comparator
8'b0111_????: begin cb_ld=1; end
// Increment
8'b0000_0110: begin acc_ld=1; cb_ld=1; end
// Decrement
8'b0000_0111: begin acc_ld=1; cb_ld=1; end
// AND
8'b0101_????: begin acc_ld=1; end

// Performing Conditional Branching, i.e. branch if carry-borrow is set.
8'b1000_????:
  if (cb)
begin
pc_l=1;
pc_in=add;
end

// Loading data from Register to Accumulator
8'b1001_????:
begin
  acc_ld=1;
  acc_next_value = data_reg; // Source for ACC is data_reg, not ALU output
end

// Storing the accumulator value to register
8'b1010_????:
begin
write=1;
data_in=acc;
end

8'b1011_????:
begin
pc_l=1;
pc_in=add;
end // RET (Assuming RET is like JMP)
8'b1111_1111: begin
  pc_l = 0; // Disabling PC update
end

```

```

        default: ; // Treat unrecognized opcodes as NOPs
    endcase
end

always @(posedge clk or posedge rst) begin
    if (rst) begin
        acc <= 8'b0;
        ext <= 8'b0;
        cb <= 1'b0;
    end else begin
        // Loading ACC from the selected source
        if (acc_ld) acc <= acc_next_value;
        if (ext_ld) ext <= alu_ext_out;
        if (cb_ld) cb <= alu_cb_out;
        // Register file write happens inside the memory module, triggered by 'write' signal only.
    end
end

endmodule

```

## **SEPARATE TESTBENCH CODES TO CHECK MODULES**

### **Testbench of ALU:**

```

module ALU_tb();

reg [7:0] opcode;
reg [7:0] acc;
reg [7:0] data_reg;
reg clk;
wire [7:0] acc_out;
wire [7:0] ext;
wire cb;

// Instantiating the ALU
ALU uut (
    .opcode(opcode),
    .acc(acc),
    .data_reg(data_reg),
    .clk(clk),
    .acc_out(acc_out),
    .ext(ext),
    .cb(cb)
);

initial begin
    clk = 0;
    forever #10 clk=~clk;
end

```

```
initial begin
```

```
// ADD
```

```
acc = 8'd10; data_reg = 8'd15; opcode = 8'b0001_0000; #10;
```

```
// SUB
```

```
acc = 8'd30; data_reg = 8'd12; opcode = 8'b0010_0000; #10;
```

```
// MUL
```

```
acc = 8'd7; data_reg = 8'd6; opcode = 8'b0011_0000; #10;
```

```
// AND
```

```
acc = 8'b11001100; data_reg = 8'b10101010; opcode = 8'b0101_0000; #10;
```

```
// XOR
```

```
acc = 8'b11001100; data_reg = 8'b10101010; opcode = 8'b0110_0000; #10;
```

```
// Comparator
```

```
acc = 8'd50; data_reg = 8'd100; opcode = 8'b0111_0000; #10;
```

```
// INC
```

```
acc = 8'd200; data_reg = 8'd0; opcode = 8'b0000_0110; #10;
```

```
// DEC
```

```
acc = 8'd100; data_reg = 8'd0; opcode = 8'b0000_0111; #10;
```

```
// LSL
```

```
acc = 8'b00001111; data_reg = 8'b0; opcode = 8'b0000_0001; #10;
```

```
// LSR
```

```
acc = 8'b11110000; data_reg = 8'b0; opcode = 8'b0000_0010;
```

```
end
```

```
endmodule
```

### **Testbench of Instruction Memory:**

```
module instruction_memory_tb();
```

```
reg [3:0] address;
```

```
wire [7:0] instruction;
```

```
// Instantiate the Instruction Memory
```

```
instruction_memory uut (.address(address), .instruct(instruction));
```

```
initial begin
```

```
address = 4'd0; #10;
```

```
address = 4'd1; #10;
```

```

address = 4'd2; #10;
address = 4'd3; #10;
address = 4'd4; #10;
address = 4'd5; #10;
address = 4'd6; #10;
address = 4'd15;
end
endmodule

```

### **Testbench of Memory(Registers):**

```

module memory_tb();

reg [7:0]data_in;
reg write , clk;
reg [3:0]address;

wire [7:0]data_out;

memory uut( .data_in(data_in) , .data_out(data_out) , .write(write), .clk(clk) , .address(address));

initial begin
clk = 0;
forever #5
clk = ~ clk;
end

initial begin
data_in = 8'd11 ; write = 0 ; address = 4'd9; #10;
data_in = 8'd19 ; write = 1 ; address = 4'd9; #10;
data_in = 8'd29 ; write = 0 ; address = 4'd9; #10;
data_in = 8'd01 ; write = 1 ; address = 4'd9; #10;
data_in = 8'd29 ; write = 1 ; address = 4'd9; #10;
data_in = 8'd9 ; write = 0 ; address = 4'd9;

end
endmodule

```

## **PROCESSOR TESTBENCH CODES**

Since in one test bench only 16 instructions can run, the other instructions are shown in the follow-up test bench [2].

### **TestBench to Show all the Instructions Running [1]**

```

module Processor_tb2();
reg clk;

```

```
reg rst;
```

```
Processor uut(  
    .clk(clk),  
    .rst(rst)  
);
```

```
initial begin  
    clk = 0;  
    forever #5 clk = ~clk;  
end
```

```
initial begin
```

```
    uut.reg_file.memo[0] = 8'd1;      // R0 = 1 (Decimal)  
    uut.reg_file.memo[1] = 8'd5;      // R1 = 5 (Decimal)  
    uut.reg_file.memo[2] = 8'd10;     // R2 = 10 (Decimal)  
    uut.reg_file.memo[3] = 8'd3;      // R3 = 3 (Decimal)  
    uut.reg_file.memo[4] = 8'd200;    // R4 = 2 (Decimal)  
    uut.reg_file.memo[5] = 8'd19;     // R5 = 19 (Decimal)  
    uut.reg_file.memo[6] = 8'd10;     // R6 = 10 (Decimal)  
    uut.reg_file.memo[7] = 8'b10101010; // R7 = 170 (Decimal) or AA (Hex)  
    uut.reg_file.memo[8] = 8'b01010101; // R8 = 85 (Decimal) or 55 (Hex)  
    uut.reg_file.memo[9] = 8'd10;     // R9 = 0  
    uut.reg_file.memo[10] = 8'd04;     // R10 = 0  
    uut.reg_file.memo[11] = 8'd20;     // R11 = 0  
    uut.reg_file.memo[12] = 8'd40;     // R12 = 0  
    uut.reg_file.memo[13] = 8'd26;     // R13 = 0  
    uut.reg_file.memo[14] = 8'd19;     // R14 = 0  
    uut.reg_file.memo[15] = 8'd16;     // R15 = 0
```

```
end
```

```
// Instruction Memory Initialization
```

```
initial begin
```

```
    uut.inst_mem.memory[0] = 8'b0000_0000;  
    uut.inst_mem.memory[1] = 8'b0001_0001;  
    uut.inst_mem.memory[2] = 8'b0010_0010;  
    uut.inst_mem.memory[3] = 8'b0011_0011;  
    uut.inst_mem.memory[4] = 8'b0101_0100;  
    uut.inst_mem.memory[5] = 8'b0110_0101;  
    uut.inst_mem.memory[6] = 8'b0111_0110;  
    uut.inst_mem.memory[7] = 8'b0000_0001;  
    uut.inst_mem.memory[8] = 8'b0000_0010;  
    uut.inst_mem.memory[9] = 8'b0000_0011;  
    uut.inst_mem.memory[10] = 8'b0000_0100;  
    uut.inst_mem.memory[11] = 8'b0000_0101;  
    uut.inst_mem.memory[12] = 8'b0000_0110;
```



```

    uut.inst_mem.memory[13] = 8'b0000_0111;
    uut.inst_mem.memory[14] = 8'b1000_0010;
    uut.inst_mem.memory[15] = 8'b1111_1111;
end

```

```

initial begin

```

```

    rst = 1;
    #10;
    rst = 0;
    #1000;
end

```

```

endmodule

```

### **TestBench to Show all the Instructions Running [2]**

```

module Processor_tb3();
reg clk;
reg rst;

```

```

Processor uut(
    .clk(clk),
    .rst(rst)
);

```

```

initial begin
    clk = 0;
    forever #5 clk = ~clk;
end

```

```

initial begin

```

```

    uut.reg_file.memo[0] = 8'd1;      // R0 = 1 (Decimal)
    uut.reg_file.memo[1] = 8'd5;      // R1 = 5 (Decimal)
    uut.reg_file.memo[2] = 8'd10;     // R2 = 10 (Decimal)
    uut.reg_file.memo[3] = 8'd3;      // R3 = 3 (Decimal)
    uut.reg_file.memo[4] = 8'd200;     // R4 = 2 (Decimal)
    uut.reg_file.memo[5] = 8'd19;     // R5 = 19 (Decimal)
    uut.reg_file.memo[6] = 8'd10;     // R6 = 10 (Decimal)
    uut.reg_file.memo[7] = 8'b10101010; // R7 = 170 (Decimal) or AA (Hex)
    uut.reg_file.memo[8] = 8'b01010101; // R8 = 85 (Decimal) or 55 (Hex)
    uut.reg_file.memo[9] = 8'd10;     // R9 = 0
    uut.reg_file.memo[10] = 8'd04;    // R10 = 0
    uut.reg_file.memo[11] = 8'd20;    // R11 = 0
    uut.reg_file.memo[12] = 8'd40;    // R12 = 0
    uut.reg_file.memo[13] = 8'd26;    // R13 = 0
    uut.reg_file.memo[14] = 8'd19;    // R14 = 0
    uut.reg_file.memo[15] = 8'd16;    // R15 = 0

```

end

// Instruction Memory Initialization

initial begin

```
uut.inst_mem.memory[0] = 8'b0000_0000;
uut.inst_mem.memory[1] = 8'b0001_0001;
uut.inst_mem.memory[2] = 8'b0010_0010;
uut.inst_mem.memory[3] = 8'b0011_0011;
uut.inst_mem.memory[4] = 8'b1010_0101;
uut.inst_mem.memory[5] = 8'b1011_0110;
uut.inst_mem.memory[6] = 8'b1000_0010;
uut.inst_mem.memory[7] = 8'b0000_0001;
uut.inst_mem.memory[8] = 8'b0000_0010;
uut.inst_mem.memory[9] = 8'b0000_0011;
uut.inst_mem.memory[10] = 8'b0000_0100;
uut.inst_mem.memory[11] = 8'b0000_0101;
uut.inst_mem.memory[12] = 8'b0000_0110;
uut.inst_mem.memory[13] = 8'b0000_0111;
uut.inst_mem.memory[14] = 8'b1000_0010;
uut.inst_mem.memory[15] = 8'b1111_1111;
```

end

initial begin

```
rst = 1;
#10;
rst = 0;
#1000;
```

end

endmodule

### **TestBench to Show Specific Program:**

module Processor\_tb();

reg clk;

reg rst;

Processor uut(

.clk(clk),

.rst(rst)

);

initial begin

clk = 0;

forever #5 clk = ~clk;

end

```

initial begin
uut.reg_file.memo[0] = 8'd1;      // R0 = 1 (Decimal)
  uut.reg_file.memo[1] = 8'd5;      // R1 = 5 (Decimal)
  uut.reg_file.memo[2] = 8'd10;     // R2 = 10 (Decimal)
  uut.reg_file.memo[3] = 8'd3;      // R3 = 3 (Decimal)
  uut.reg_file.memo[4] = 8'd200;     // R4 = 2 (Decimal)
  uut.reg_file.memo[5] = 8'd19;     // R5 = 19 (Decimal)
  uut.reg_file.memo[6] = 8'd10;     // R6 = 10 (Decimal)
  uut.reg_file.memo[7] = 8'b10101010; // R7 = 170 (Decimal) or AA (Hex)
  uut.reg_file.memo[8] = 8'b01010101; // R8 = 85 (Decimal) or 55 (Hex)
  uut.reg_file.memo[9] = 8'd10;     // R9 = 0
  uut.reg_file.memo[10] = 8'd04;     // R10 = 0
  uut.reg_file.memo[11] = 8'd20;     // R11 = 0
  uut.reg_file.memo[12] = 8'd40;     // R12 = 0
  uut.reg_file.memo[13] = 8'd26;     // R13 = 0
  uut.reg_file.memo[14] = 8'd19;     // R14 = 0
  uut.reg_file.memo[15] = 8'd16;     // R15 = 0
end

```

end

// Instruction Memory Initialization

```

initial begin
  uut.inst_mem.memory[0] = 8'b1001_0001; // ADD R1    -> ACC = ACC + R1
  uut.inst_mem.memory[1] = 8'b0001_0010; // SUB R2    -> ACC = ACC - R2
  uut.inst_mem.memory[2] = 8'b0010_0011; // MOV ACC, R3 -> ACC = R3
  uut.inst_mem.memory[3] = 8'b0011_0100; // MOV R4, ACC -> R4 = ACC
  uut.inst_mem.memory[4] = 8'b1000_0011; // XRA R5     -> ACC ^= R5
  uut.inst_mem.memory[5] = 8'b1111_1111; // BR R9      -> if CB = 1, jump to R9
  uut.inst_mem.memory[6] = 8'b0000_0000; // HLT       -> Stop execution
  uut.inst_mem.memory[7] = 8'b0000_0000;
  uut.inst_mem.memory[8] = 8'b0000_0000;
  uut.inst_mem.memory[9] = 8'b0000_0000;
  uut.inst_mem.memory[10] = 8'b0000_0000;
  uut.inst_mem.memory[11] = 8'b0000_0000;
  uut.inst_mem.memory[12] = 8'b0000_0000;
  uut.inst_mem.memory[13] = 8'b0000_0000;
  uut.inst_mem.memory[14] = 8'b0000_0000;
  uut.inst_mem.memory[15] = 8'b0000_0000;
end

```

end

initial begin

```

  rst = 1;
  #10;
  rst = 0;
  #1000;


```

end


endmodule

# SIMULATION RESULTS


## Memory (Register) Testbench

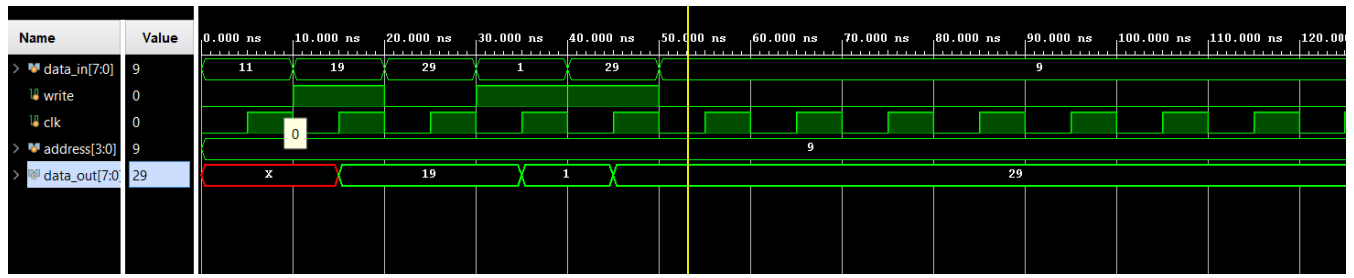


## Instruction Memory Testbench

 


## ALU Testbench

 

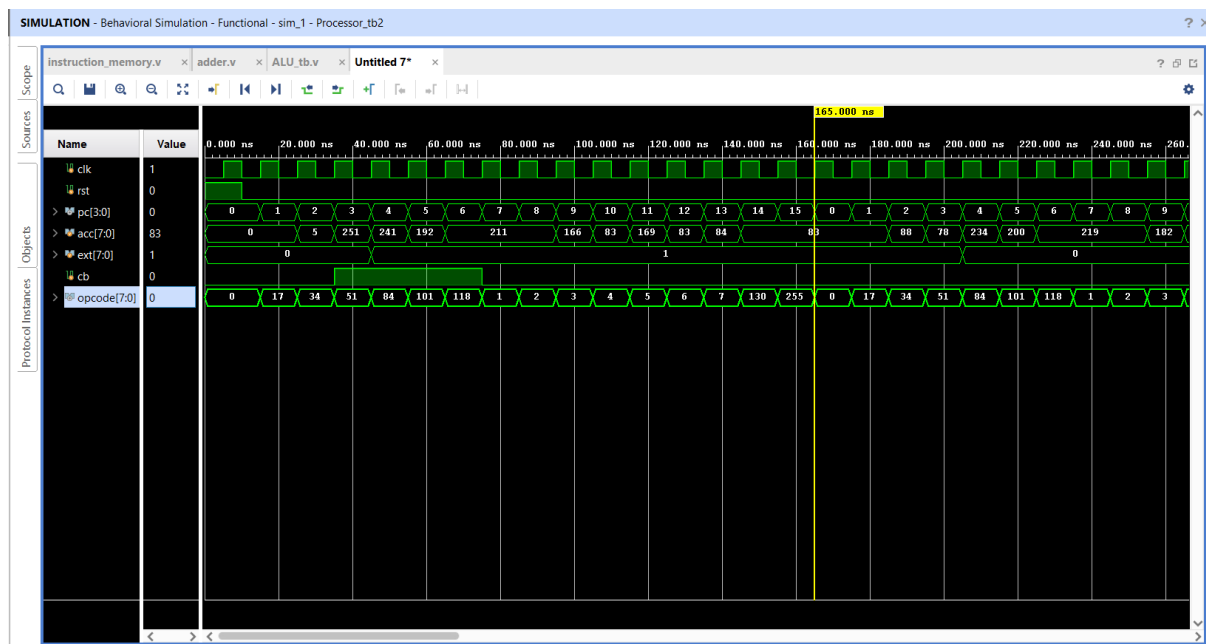
## Main Testbench Showing All Instructions




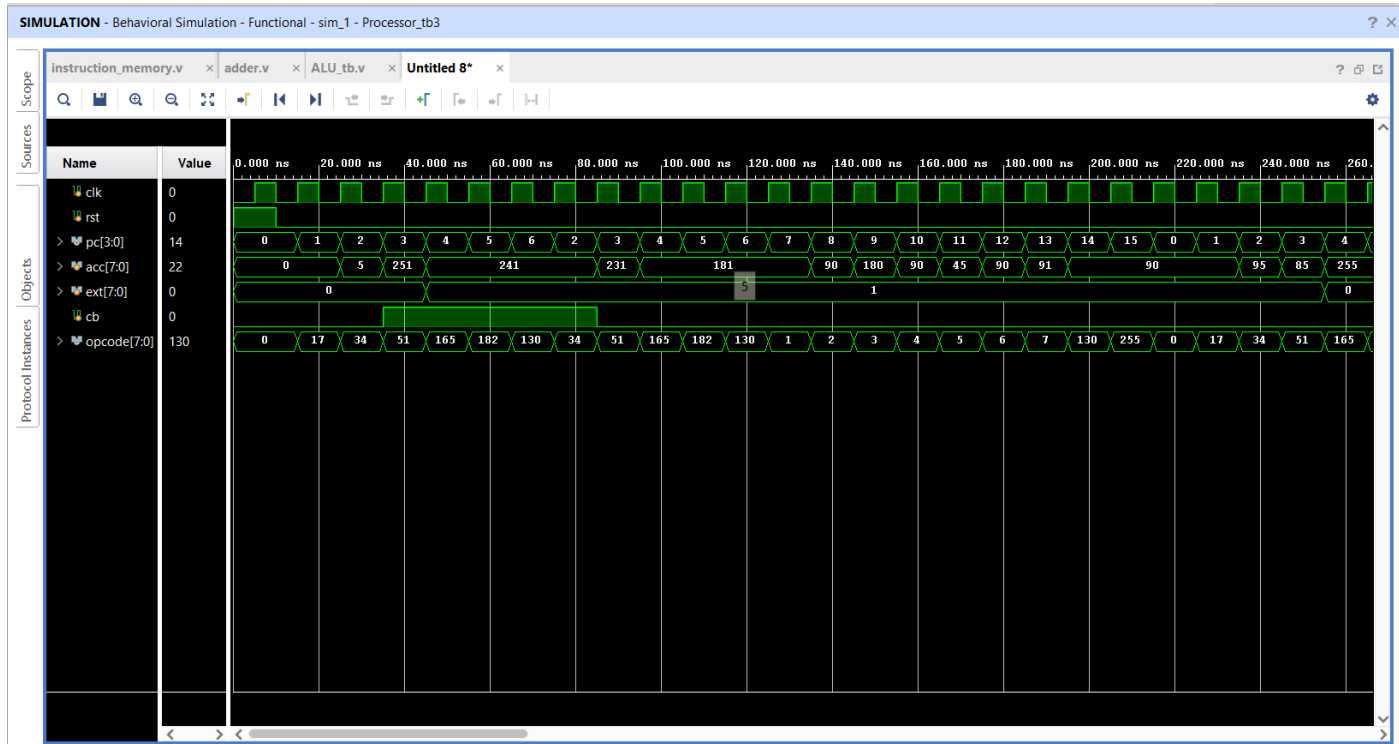


## Simulation for Specific Program

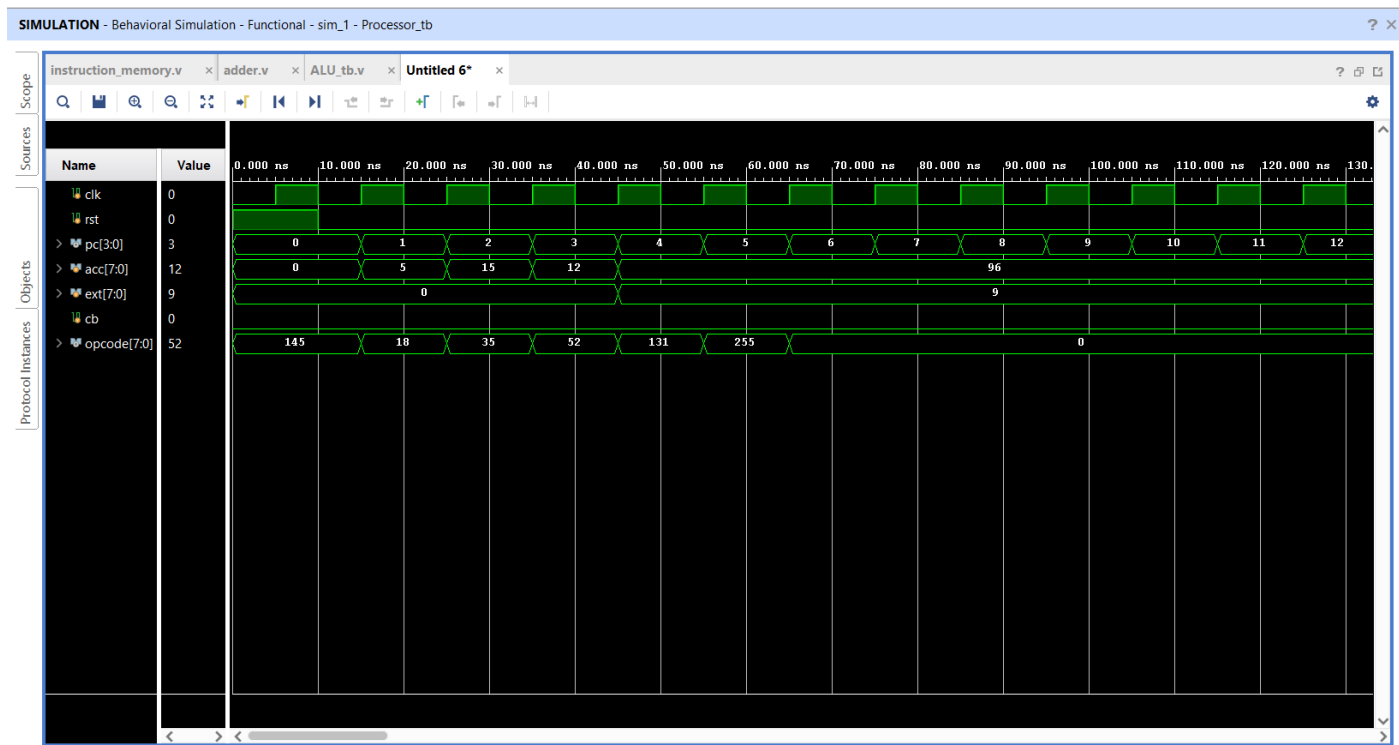

## BLOCK DIAGRAM

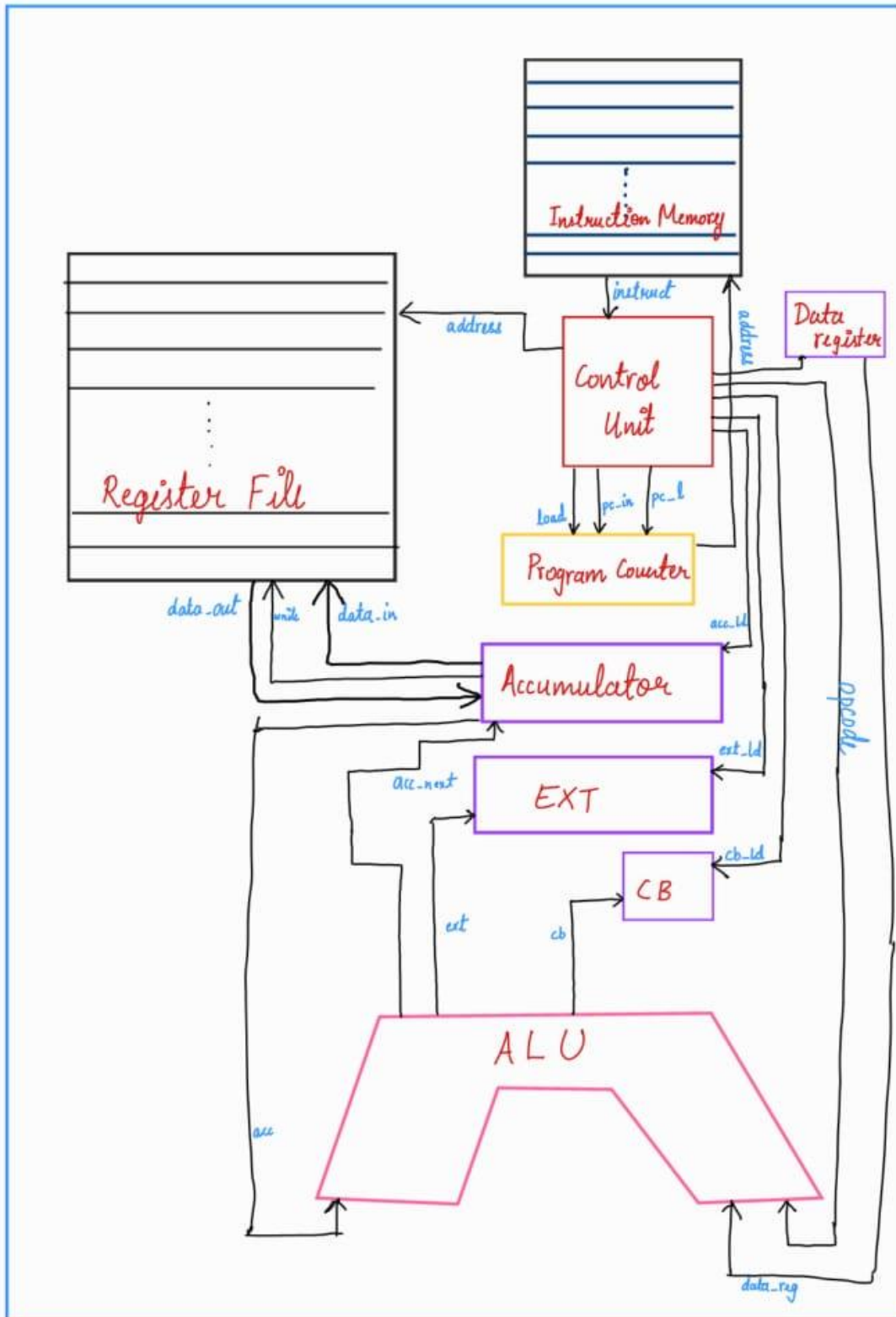

## SCHEMATIC OF THE PROCESSOR

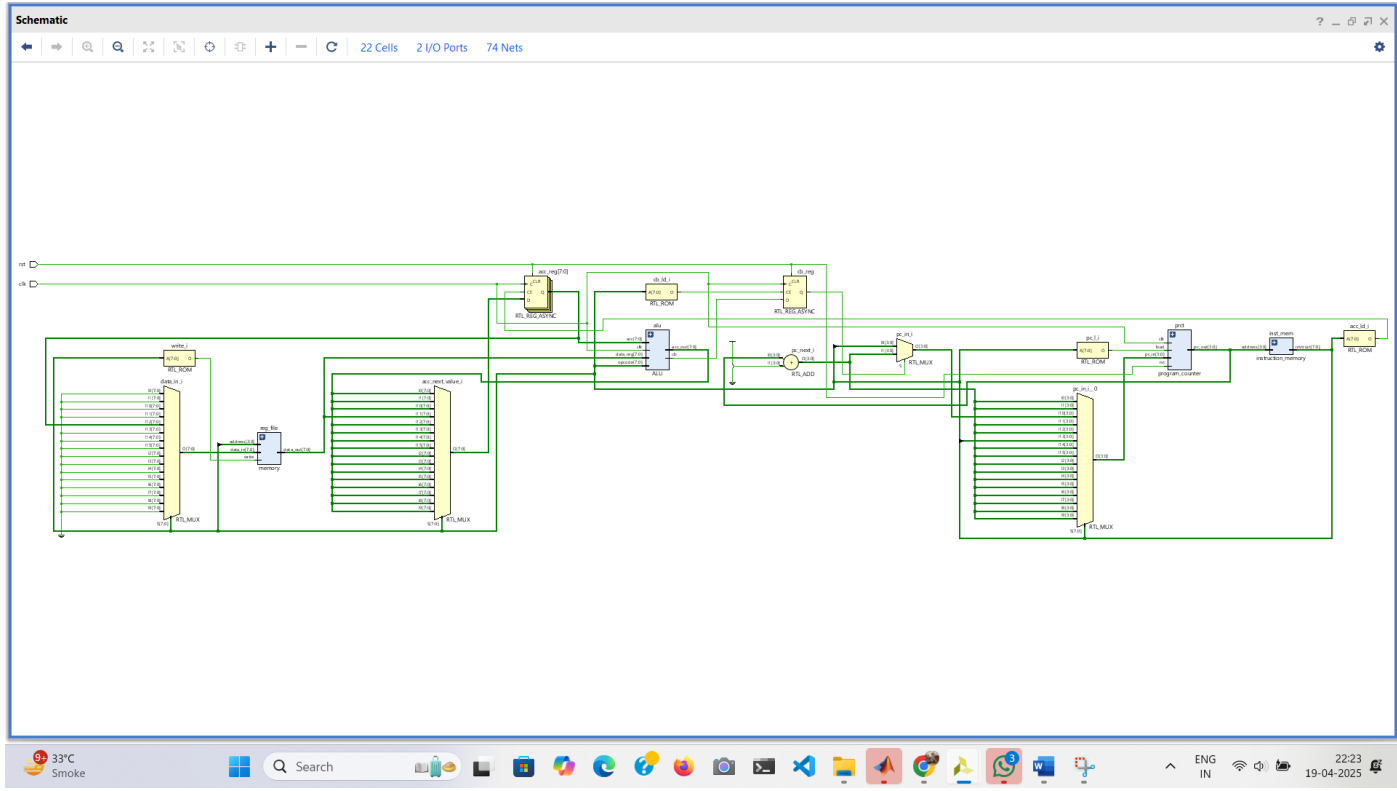

## Zoomed in views

